
Polyphonic Digital Synth

Teenage Mixing Ninja Turtles

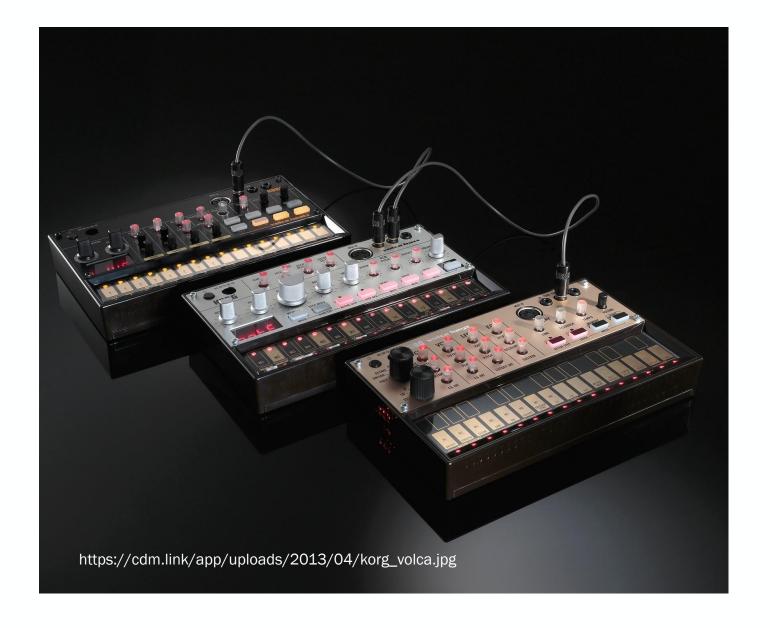

Goal of the Design


- The project aims to replicate a basic synth that has multiple button inputs and can produce unique tones with each button press, while also allowing for polyphonic mixing.
- The team's design will have 12 buttons that can be mixed to represent a full scale.
- The final product will generate a PWM wave that will be played through a speaker with a DAC.






Overall User Flow Diagram

Sound Generation Sequence

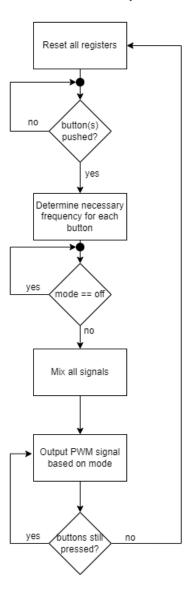


Mode Select

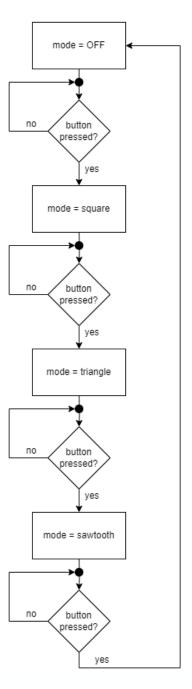





Overview

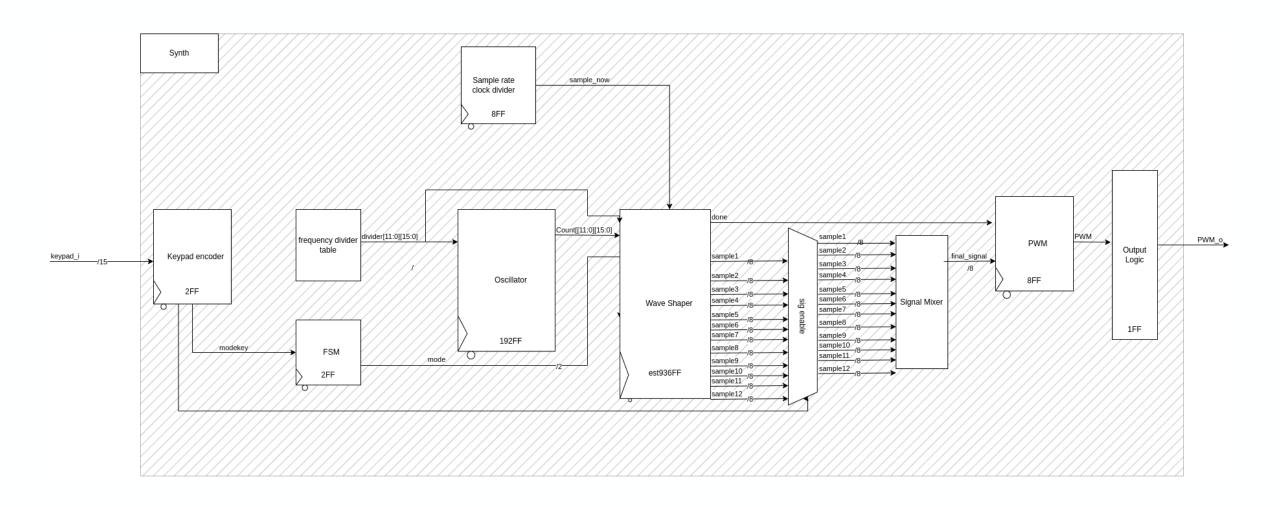

Keypad

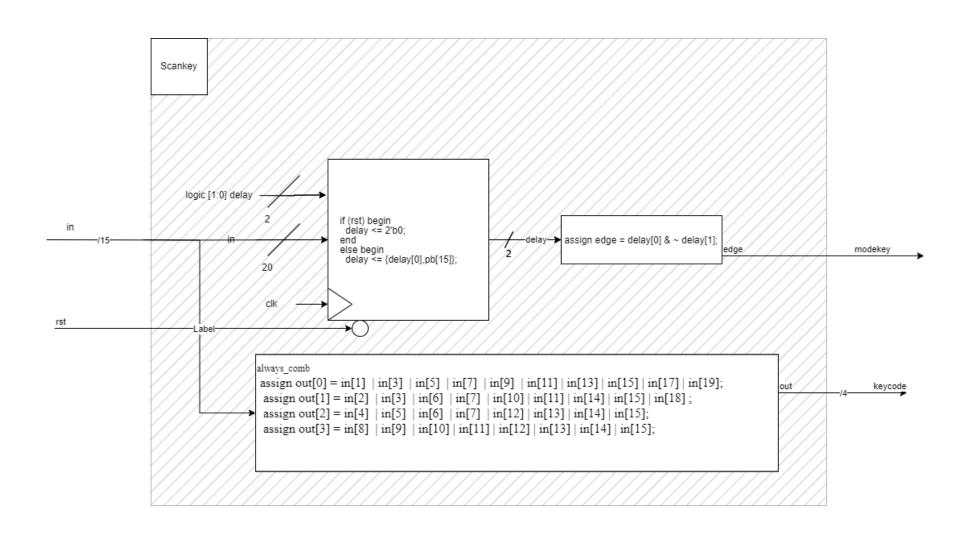


Keypad

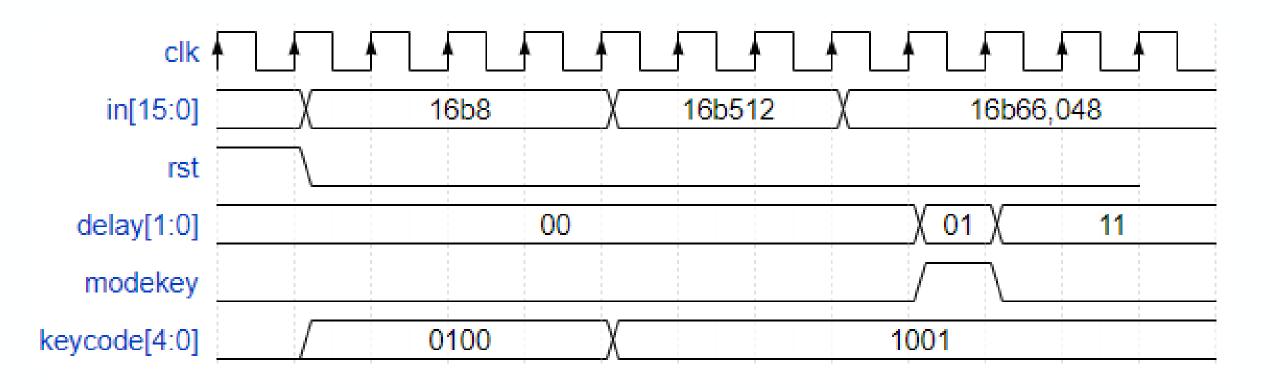


FSM

State Diagram

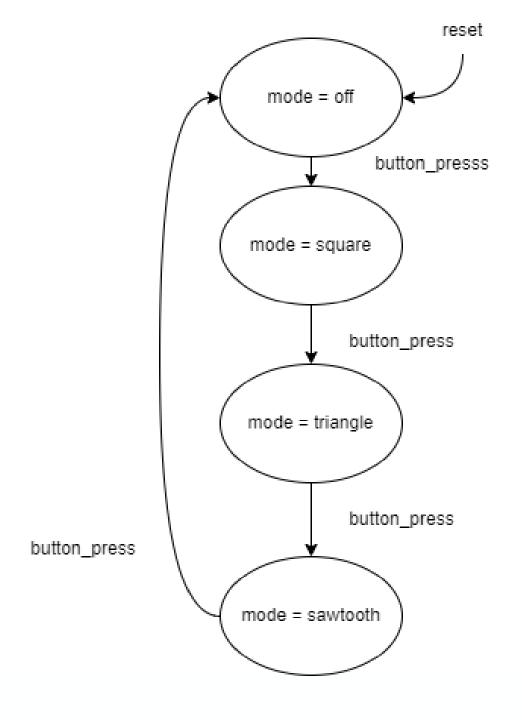


FSM


Register Transfer Level

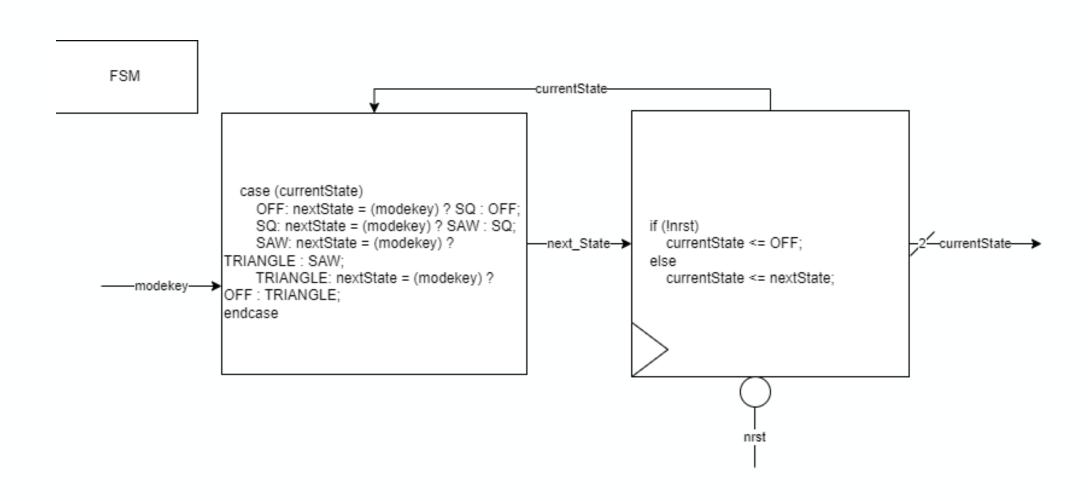


Oscillator

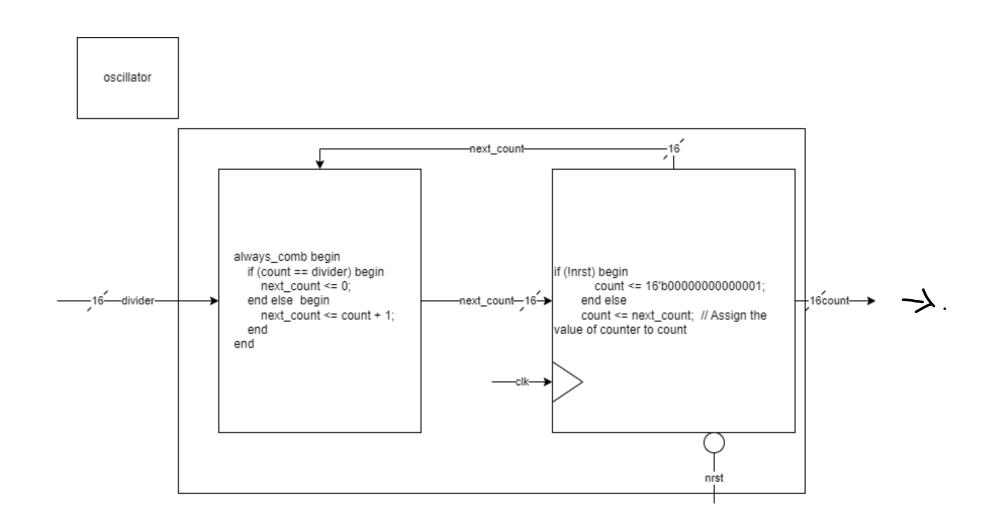

Oscillator

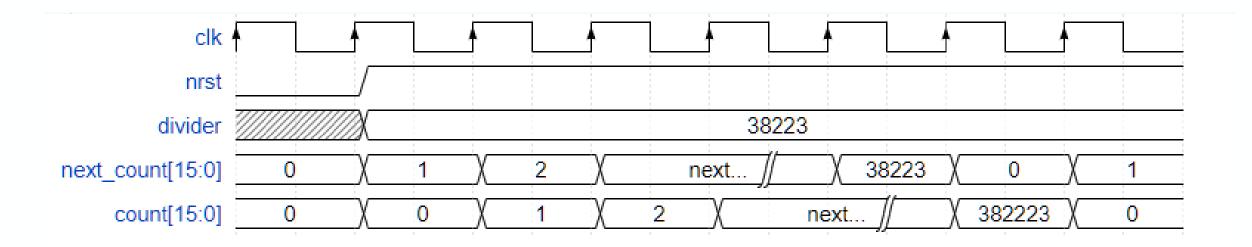


Sample Rate ClkDiv

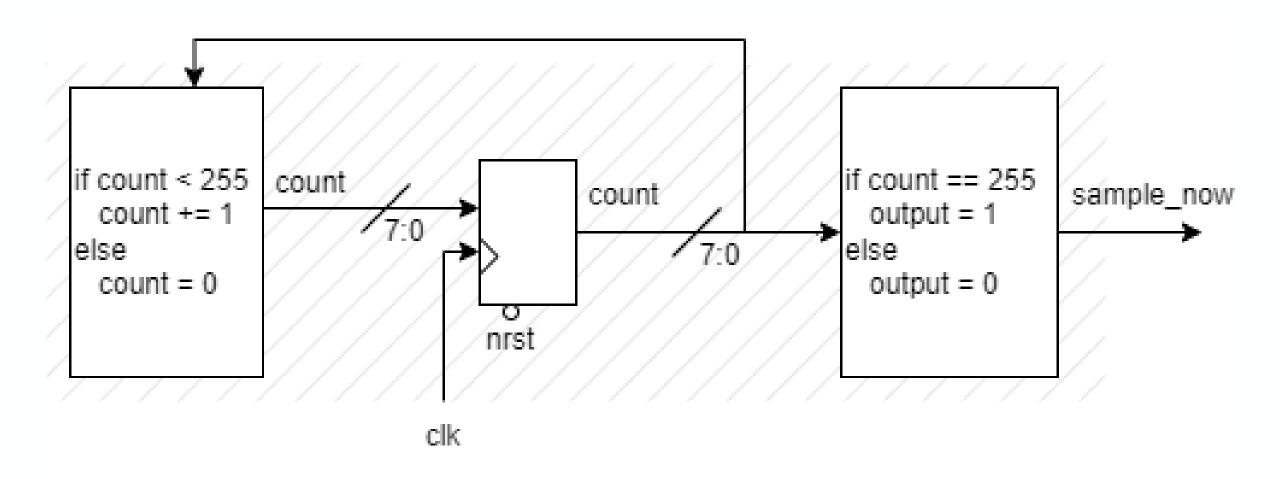

Sample Rate ClkDiv


Wavedrom

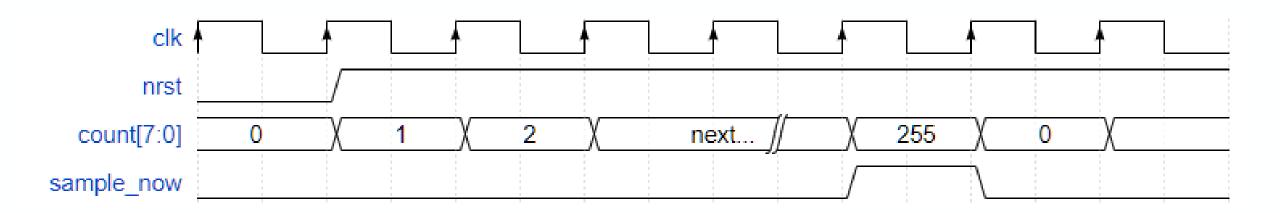




Wave Shaper

RTL

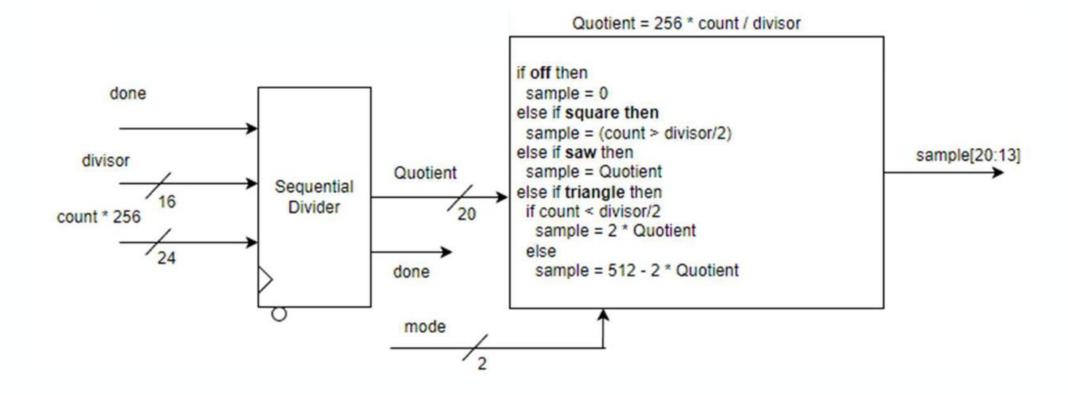


Wave Shaper sub-RTL

Sequential divider

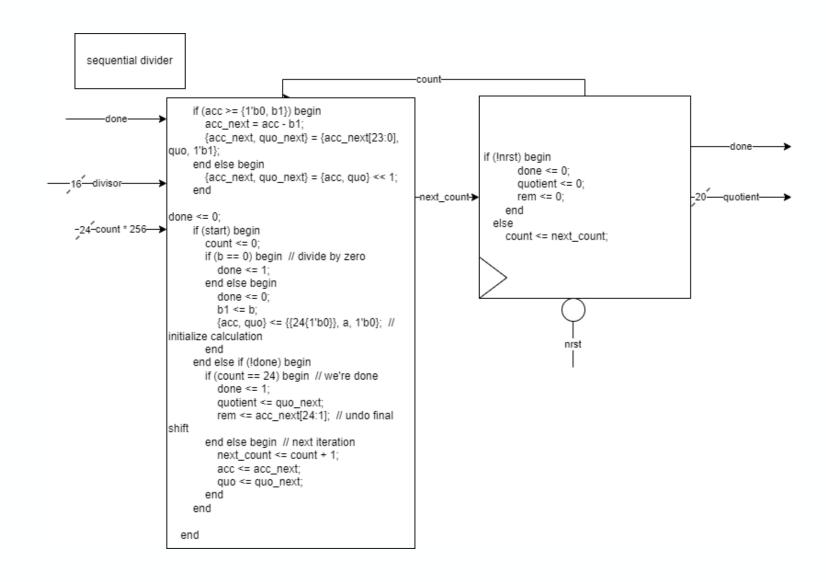


Wavedrom

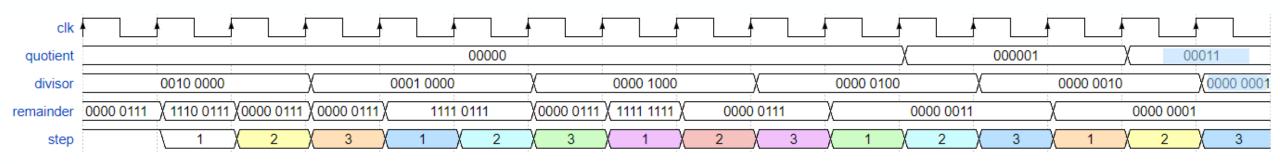

Wave Shaper

RTL

Signal Mixer

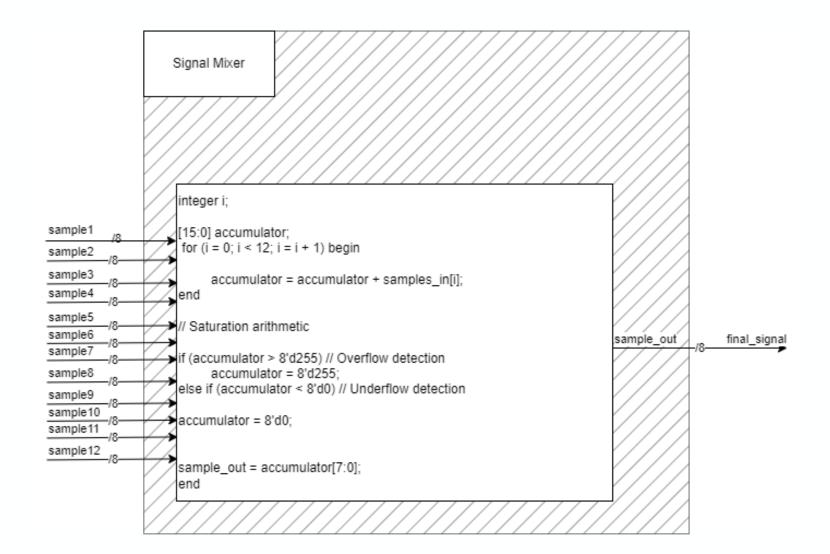


Wavedrom

Signal Mixer

samples_in[0]	0		0	X	255	
samples_in[1]	0		2		255	
samples_in[2]	0		35		255	
samples_in[3]	0		2		255	
samples_in[4]	0		10		255	
samples_in[5]	0		9		255	
samples_in[6]	0		2		255	
samples_in[7]	0		13	X	255	
samples_in[8]	0		8		255	
samples_in[9]	0		16		255	
samples_in[10]	0		3		255	
samples_in[11]	0		4		255	
accumulator[15:0]	0	X	104	X	3060	
sample_out	0	X	104	X	255	


RTL

PWM

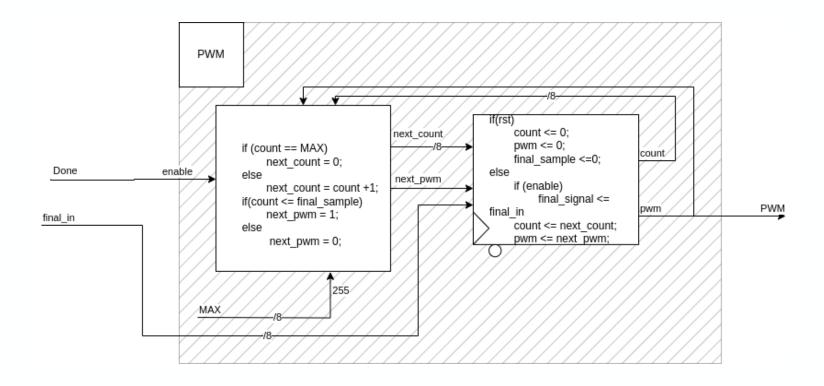

Wavedrom

PWM

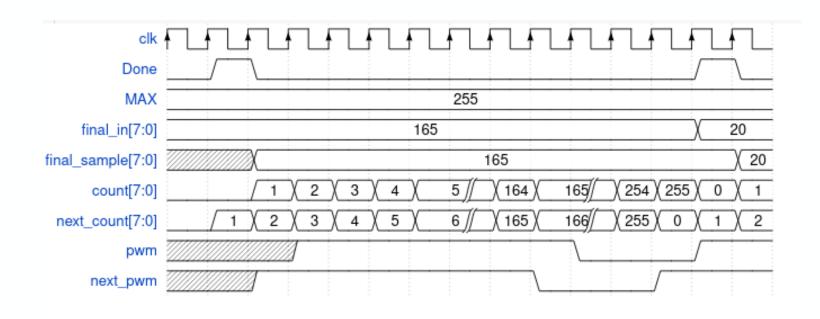

Number of Flip-Flops

Module	Number of Flip-Flops		
Keypad	2		
Frequency Divider Table	2		
FSM	2		
Oscillator	192		
Sample ClkDiv	2		
Wave Shaper	938		
Signal Mixer	0		
PWM	8		
Logic Out	1		
Total	1147		

I/O Pins

1/0	Number of pins	Component
Keypad (notes)	12	Push Button
Reset	1	Push Button
Mode	1	Push Button
PWM_out	1	Speaker
Total	15	